

2003 silverado radio wiring diagram

2003 Silverado Radio Wiring Diagram: A Detailed Guide for Your Installation Needs

2003 silverado radio wiring diagram is a crucial resource for anyone looking to upgrade, repair, or replace the factory radio system in their Chevrolet Silverado truck. Whether you're a seasoned car audio enthusiast or a first-time installer, understanding the wiring layout can make the process smoother and help avoid costly mistakes. The 2003 Silverado, part of the Silverado 1500 series, has a specific wiring configuration that supports the stock radio and aftermarket upgrades, so having the right wiring diagram at hand is invaluable.

In this article, we'll explore the ins and outs of the 2003 Silverado radio wiring diagram, including key wire colors, harness connections, and tips on integrating aftermarket stereos. We'll also touch on related concepts like speaker wiring, power connections, and antenna adapters to ensure you have a comprehensive understanding before you dive into your project.

Understanding the Basics of the 2003 Silverado Radio Wiring Diagram

Before you start unplugging wires or cutting into your dash, it's important to grasp the fundamentals of the radio wiring system in the 2003 Silverado. The radio wiring harness acts as the central hub, connecting power, speakers, antennas, and controls to the stereo unit.

What Does the Wiring Diagram Show?

A wiring diagram is essentially a map that details the electrical connections and color codes for each wire within the system. For the 2003 Silverado, the diagram typically includes:

- **Power wires:** These supply the necessary voltage for the radio to function.
- **Ground wires:** Essential for completing the electrical circuit and preventing noise.
- **Speaker wires:** Carry the audio signals to your truck's speakers.
- **Antenna power:** Powers the antenna amplifier if equipped.
- **Illumination and dimmer wires:** Adjust the radio display brightness based on lighting conditions.

Having access to this diagram helps you identify which wire is which, allowing proper connections without guesswork.

Key Wire Colors and Their Functions

One of the most helpful aspects of the 2003 Silverado radio wiring diagram is the standardized color coding. While variations might exist depending on trim and optional packages, here's a general guide to the wire colors you can expect:

- **Yellow:** Constant 12V power (battery)
- **Red:** Switched 12V power (ignition)
- **Black:** Ground
- **Blue:** Antenna power or amplifier turn-on
- **Orange:** Illumination/dimmer
- **White and White with black stripe:** Front left speaker (+ and -)
- **Gray and Gray with black stripe:** Front right speaker (+ and -)
- **Green and Green with black stripe:** Rear left speaker (+ and -)
- **Purple and Purple with black stripe:** Rear right speaker (+ and -)

Knowing these colors lets you quickly match wires when installing an aftermarket radio or troubleshooting your current system.

How to Use the 2003 Silverado Radio Wiring Diagram for Aftermarket Stereo Installation

Upgrading your truck's radio is a popular modification, and having the factory wiring diagram at hand can save hours of frustration. Here are some tips on using the diagram effectively during an installation:

Step 1: Identify Your Vehicle's Wiring Harness

The first step is locating the factory radio harness behind the dashboard. The 2003 Silverado uses a standardized connector, which makes it compatible with many aftermarket harness adapters. These adapters essentially plug into the factory harness and allow you to connect the aftermarket radio without cutting wires.

Step 2: Match the Wires Using the Diagram

Using the wiring diagram, carefully identify the corresponding wires on the aftermarket harness adapter. Most manufacturers provide color-coded wires that match the factory colors, but it's always good practice to verify with a multimeter or test light before making connections.

Step 3: Connect Securely and Insulate

Once you've matched the wires, use soldering or crimp connectors to join them securely. Proper insulation with electrical tape or heat shrink tubing is essential to prevent shorts or corrosion.

Step 4: Test Before Final Assembly

Before reassembling your dashboard, turn on the ignition and test the radio to ensure power, sound, and controls function correctly. Confirm that all speakers are producing sound and that features like illumination and antenna power work as expected.

Common Challenges and Troubleshooting Tips

Even with a wiring diagram, some hurdles can appear during installation. Here are a few common issues and how to address them:

- **No power to the radio:** Verify the yellow (constant power) and red (switched power) wires. Check fuses and ground connections.
- **No sound from speakers:** Double-check speaker wire polarity and connections. Make sure the head unit is compatible with the speaker system.
- **Radio display doesn't dim:** Ensure the orange illumination wire is connected and receiving power from the dash lighting circuit.
- **Antenna doesn't work:** Confirm the blue antenna wire is connected if your vehicle uses an amplified antenna.

Additional Components Related to the 2003 Silverado Radio Wiring Diagram

Understanding the radio wiring diagram also involves being aware of supplementary parts that impact your audio setup.

Factory Amplifier and Speaker Wiring

Many 2003 Silverado models come equipped with a factory amplifier, especially in higher trims or models with premium sound packages. In these cases, the wiring diagram will include additional connectors and wires that run from the head unit to the amplifier and then out to the speakers.

When installing an aftermarket radio in a Silverado with a factory amplifier, you may need a special adapter or bypass harness to ensure compatibility. Some aftermarket units can integrate directly, while others require the amplifier to be bypassed or replaced.

Antenna and Signal Connections

The antenna wiring in the 2003 Silverado isn't just a simple coaxial cable; it often includes a power wire to activate the antenna amplifier. The wiring diagram shows the blue wire dedicated to this function, which must be connected correctly for optimal radio reception.

If you're upgrading to a radio with different antenna input requirements, you may need an adapter or signal converter to maintain good reception quality.

Using Wiring Harness Adapters for a Clean Installation

One of the easiest ways to simplify the installation process is to use a vehicle-specific wiring harness adapter. These adapters plug directly into the 2003 Silverado's factory harness, eliminating the need to cut or splice factory wires. They also maintain the integrity of your truck's electrical system and make it easier to revert to the original radio if desired.

Purchasing a quality adapter designed for the 2003 Silverado model ensures that wire colors and functions correspond correctly, making the installation process more straightforward and less prone to errors.

Why Having the 2003 Silverado Radio Wiring Diagram Matters

Many people underestimate the importance of having an accurate wiring diagram when working on their vehicle's audio system. Without it, you risk damaging wires, blowing fuses, or worse, creating electrical shorts that could affect other vehicle systems.

The wiring diagram acts as a roadmap, providing clarity and confidence during installation or troubleshooting. It also saves time by reducing guesswork, which can be especially valuable if you're integrating components like amplifiers, subwoofers, or steering wheel controls.

By understanding the intricacies of the 2003 Silverado's radio wiring layout, you're better equipped to make modifications that enhance your driving experience without compromising safety or reliability.

Additional Tips for a Successful Radio Upgrade

- **Label your wires:** Even if the colors are standardized, labeling wires during disassembly helps prevent confusion.
- **Consult online forums:** Silverado owner communities often share wiring diagrams, installation tips, and product recommendations.
- **Use quality tools:** A digital multimeter, wire strippers, and crimpers will make your job easier and more professional-looking.
- **Keep factory wiring intact:** Preserve the factory wiring as much as possible to maintain resale value and ease of future repairs.
- **Consider professional help:** If you're unsure about your skills, a professional car audio installer can leverage the wiring diagram to ensure a perfect setup.

Navigating the complexities of vehicle wiring can seem daunting at first, but with resources like the 2003 Silverado radio wiring diagram and a patient approach, upgrading your truck's audio system becomes an achievable and rewarding project. Whether you're enhancing sound quality, adding Bluetooth connectivity, or installing a touchscreen display, this diagram is your essential guide to a smooth and successful installation.

Frequently Asked Questions

Where can I find a 2003 Silverado radio wiring diagram?

You can find the 2003 Silverado radio wiring diagram in the vehicle's service manual, online automotive forums, or websites specializing in wiring diagrams such as AutoZone or RepairPal.

What colors are the 2003 Silverado radio wiring harness wires?

Common wire colors for the 2003 Silverado radio wiring harness include yellow (constant 12V), red (switched 12V), black (ground), blue (antenna/power antenna), and various speaker wires which are typically white, gray, green, and purple with positive and negative leads.

How do I connect an aftermarket radio to a 2003 Silverado?

To connect an aftermarket radio, use a wiring harness adapter specific to the 2003 Silverado to avoid cutting factory wires. Match the adapter's wire colors to the aftermarket radio wires (power, ground, speakers), and use crimp connectors or solder for secure connections.

Does the 2003 Silverado have a separate amplifier wiring for the radio?

Some 2003 Silverado models equipped with premium sound systems may have a separate amplifier. The radio wiring diagram will show an amplifier turn-on wire (usually blue with a white stripe) that needs to be connected to the aftermarket amplifier's remote turn-on lead.

What is the wire for the antenna in the 2003 Silverado radio wiring?

The antenna power wire in the 2003 Silverado is typically a blue wire, which supplies 12V to power the power antenna or amplifier turn-on signal.

How can I identify the speaker wires in the 2003 Silverado radio wiring diagram?

Speaker wires in the 2003 Silverado are color-coded in pairs, with a positive and negative wire for each speaker. For example, front left speaker wires might be white (positive) and white with black stripe (negative), while rear speakers use green and purple pairs.

Is the ignition-switched power wire in the 2003 Silverado radio wiring red?

Yes, the ignition-switched power wire in the 2003 Silverado radio wiring harness is typically red. It provides power only when the ignition is in the accessory or run position.

Can I use a universal wiring diagram for the 2003 Silverado radio?

While some universal wiring diagrams may provide general guidance, it's best to use a wiring diagram specific to the 2003 Silverado to ensure proper wire identification and avoid damage to the vehicle's electrical system.

What tools do I need to install a radio in a 2003 Silverado using the wiring diagram?

You'll need basic tools such as wire strippers, crimp connectors or soldering tools, electrical tape, a multimeter for testing wires, and a wiring harness adapter specific to the 2003 Silverado for a clean installation.

How do I troubleshoot radio wiring issues in a 2003 Silverado?

To troubleshoot, first check the fuse related to the radio, then use a multimeter to verify power and ground wires are delivering proper voltage. Consult the wiring diagram to ensure all connections match the correct wires and check for any damaged or loose wiring.

Additional Resources

2003 Silverado Radio Wiring Diagram: A Comprehensive Guide for Installation and Troubleshooting

2003 silverado radio wiring diagram serves as an essential reference for vehicle owners, audio technicians, and DIY enthusiasts aiming to install, upgrade, or repair the factory or aftermarket audio systems in Chevrolet Silverado trucks. Understanding the intricate wiring layout of the 2003 Silverado radio system facilitates accurate connections, prevents electrical faults, and enhances the overall audio experience. This article delves into the specifics of the 2003 Silverado radio wiring diagram, offering a detailed analysis of the wiring harnesses, color codes, and compatibility considerations that are crucial for seamless integration and troubleshooting.

Understanding the 2003 Silverado Radio Wiring Diagram

The 2003 Chevrolet Silverado, a full-size pickup truck, features a factory-installed audio system designed to work harmoniously with the vehicle's electrical architecture. The radio wiring diagram for this model outlines the connections between the radio head unit, power sources, speakers, antenna, and accessory controls. Grasping these details is vital for anyone seeking to install an aftermarket radio or repair the existing system without causing damage to the vehicle's electrical components.

The 2003 Silverado radio wiring diagram typically includes two main harnesses: the primary radio connector and the speaker wiring harness. The primary connector manages power inputs and outputs, including constant 12V power, switched ignition power, ground, illumination, and antenna

control. The speaker harness, on the other hand, handles the left and right front and rear speaker connections.

Key Components and Wiring Functions

To navigate the 2003 Silverado radio wiring diagram effectively, understanding the purpose of each wire and connector is imperative:

- **Constant 12V Power (Yellow Wire):** Supplies continuous power to retain radio memory settings.
- **Switched Ignition Power (Red Wire):** Powers the radio only when the ignition is on.
- **Ground (Black Wire):** Provides electrical grounding for the radio unit.
- **Illumination (Orange Wire):** Connects to the vehicle's dimmer switch to adjust radio display brightness.
- **Antenna Control (Blue Wire):** Activates the power antenna or amplifier when the radio is turned on.
- **Speaker Wires:** Typically color-coded in pairs for positive and negative terminals for each speaker: front left, front right, rear left, rear right.

These standardized color codes align with General Motors' wiring conventions for the early 2000s, making the 2003 Silverado radio wiring diagram applicable across various Silverado trims and similar GM models.

Installation Considerations When Using the 2003 Silverado Radio Wiring Diagram

When installing an aftermarket radio in a 2003 Silverado, referencing the factory wiring diagram is crucial to ensure compatibility and prevent electrical issues. The diagram assists in identifying which wires correspond to power, ground, speakers, and other functions, thereby reducing the risk of reversed speaker polarity or blown fuses.

Many vehicle owners opt to use wiring harness adapters designed specifically for the 2003 Silverado. These adapters plug directly into the factory harness and the aftermarket radio, preserving the vehicle's wiring integrity and simplifying installation. However, understanding the underlying wiring diagram remains valuable, especially for troubleshooting or custom installations.

Common Challenges and Solutions

- **Speaker Wire Identification:** Without the wiring diagram, misidentifying speaker wires can lead to poor sound quality or no audio output. The diagram clarifies which wires correspond to which speakers and their polarity.
- **Power Wire Confusion:** Differentiating the constant 12V power from the switched ignition power is essential to avoid battery drain. The diagram highlights these distinctions clearly.
- **Illumination and Antenna Wire Integration:** Some aftermarket radios may not support illumination dimming or power antenna control. The wiring diagram helps identify these wires so they can be safely capped or repurposed.

Comparing 2003 Silverado Radio Wiring with Other Model Years

While the 2003 Silverado shares many wiring characteristics with its early 2000s counterparts, subtle differences exist between model years that affect radio wiring compatibility. For instance, Silverado models manufactured before 2002 may have different connector types or wire color schemes, and those produced after 2004 might include additional features such as satellite radio or amplified audio systems requiring extra wiring.

The 2003 Silverado radio wiring diagram reflects a transitional period where factory systems began incorporating more sophisticated controls but retained the basic GM wiring color standards. When upgrading or repairing radios in this model year, cross-referencing the 2003 diagram with adjacent years ensures compatibility and prevents miswiring.

Aftermarket vs. Factory Wiring Harnesses

An important consideration for users working with the 2003 Silverado radio wiring diagram is whether to retain the factory wiring harness or replace it with an aftermarket alternative. Factory harnesses are designed specifically for the vehicle's electrical system but may complicate installation if modifications are needed.

Aftermarket harnesses, often sold with universal or vehicle-specific adapters, offer simplified connections with color-coded leads matching standard aftermarket head unit wiring. However, they may omit some factory features such as steering wheel controls or amplifier interfaces, which require additional adapters or modules.

Technical Specifications and Wire Color Codes in the 2003 Silverado Wiring Diagram

Understanding the technical specifications associated with each wire in the 2003 Silverado radio wiring diagram helps ensure correct installation and system functionality. Below is a detailed overview of the common wires and their functions:

1. **Yellow - Constant 12V (+):** Maintains memory functions such as presets and clock.
2. **Red - Switched 12V (+):** Powers the radio when the ignition is turned on.
3. **Black - Ground (-):** Connects to the vehicle chassis ground.
4. **Orange - Illumination/Dimmer (+):** Adjusts radio display brightness corresponding to dashboard lighting.
5. **Blue - Power Antenna/Amplifier Remote (+):** Activates external amplifiers or power antenna.
6. **Speaker Wires:** Usually paired with one solid color wire and one wire with a stripe; for example, white (front left positive) and white/black (front left negative).

These wire colors align with GM's standard wiring practices, enabling easier identification and connection during installations or repairs.

Speaker Wire Color Coding

- Front Left: White (+), White/Black (-)
- Front Right: Gray (+), Gray/Black (-)
- Rear Left: Green (+), Green/Black (-)
- Rear Right: Purple (+), Purple/Black (-)

Maintaining correct polarity is vital for optimal sound staging and to avoid phase cancellation, which can degrade audio quality.

Using the 2003 Silverado Radio Wiring Diagram for Troubleshooting

Beyond installation, the 2003 Silverado radio wiring diagram is an indispensable tool for diagnosing audio system issues. Common problems such as no power to the radio, intermittent audio, or one-sided speaker output can often be traced to wiring faults revealed by the diagram.

For example, if the radio does not turn on, technicians can verify the presence of 12V power on the red and yellow wires and confirm a proper ground connection on the black wire. Similarly, if certain speakers fail to produce sound, the diagram helps isolate which wires to test for continuity or shorts.

Additionally, the diagram assists in identifying whether the antenna control wire is properly supplying voltage to the power antenna motor or amplifier remote, resolving reception issues.

Tools and Techniques for Effective Use

Using the wiring diagram effectively requires appropriate tools such as a multimeter, wire strippers, crimpers, and electrical tape. A multimeter enables measurement of voltage, resistance, and continuity, essential for verifying wire functions and integrity.

Moreover, labeling wires during disassembly and carefully following the wiring diagram prevents confusion, especially when dealing with similar wire colors or multiple connectors.

Conclusion

The 2003 Silverado radio wiring diagram is a critical resource for anyone involved in the installation, upgrade, or repair of the Silverado's audio system. By providing detailed insights into wire functions, color codes, and connector layouts, the diagram enhances accuracy, efficiency, and safety during electrical work. Whether integrating an aftermarket radio, troubleshooting system malfunctions, or preserving factory features, leveraging the wiring diagram ensures a professional and reliable outcome tailored to the 2003 Silverado's unique specifications.

[2003 Silverado Radio Wiring Diagram](#)

Find other PDF articles:

<https://lxc.avoiciformen.com/archive-top3-18/files?docid=PKq33-9773&title=lost-tribes-and-promise-d-lands-pdf.pdf>

36 years, millions of consumers have turned to Edmunds' price guides for their car shopping needs. Edmunds' New Cars & Trucks guides include up-to-date dealer invoice and MSRP pricing for all new vehicles, reviews on more than 230 models and buying advice to help you make informed decisions on your new car or truck purchase.

2003 silverado radio wiring diagram: The 4x4'S, Pickups and Vans Buying Guide 2003 Consumer Guide, 2003-03 Updated for 2003, this comprehensive guide contains profiles of more than 60 new sport-utility vehicles, pickup trucks, and vans, with complete specifications on cargo dimensions and payloads, plus hands-on reviews, up-to-date prices, and more.

2003 silverado radio wiring diagram: Popular Science , 2004-09 Popular Science gives our readers the information and tools to improve their technology and their world. The core belief that Popular Science and our readers share: The future is going to be better, and science and technology are the driving forces that will help make it better.

2003 silverado radio wiring diagram: Popular Science , 2007-05 Popular Science gives our readers the information and tools to improve their technology and their world. The core belief that Popular Science and our readers share: The future is going to be better, and science and technology are the driving forces that will help make it better.

2003 silverado radio wiring diagram: F&S Index United States Annual , 1999

2003 silverado radio wiring diagram: Popular Science , 2001-12 Popular Science gives our readers the information and tools to improve their technology and their world. The core belief that Popular Science and our readers share: The future is going to be better, and science and technology are the driving forces that will help make it better.

2003 silverado radio wiring diagram: EDN , 1975

2003 silverado radio wiring diagram: Low Rider , 2003

2003 silverado radio wiring diagram: Ward's Business Directory of U.S. Private and Public Companies , 2007 This multi-volume set is a primary source for basic company and industry information. Names, addreses, SIC code, and geographic location of over 135,000 U.S. companies are included.

2003 silverado radio wiring diagram: 4x4s, Pickups and Vans Consumer Guide, 2002-04 An invaluable resource for shoppers in the fastest growing segment of the new-vehicle market, this reference provides information on the best buys, up-to-date prices, hands-on reviews, and shopping tips, and features profiles on more than 60 new sport-utility vehicles.

2003 silverado radio wiring diagram: Los Angeles Magazine , 2003-11 Los Angeles magazine is a regional magazine of national stature. Our combination of award-winning feature writing, investigative reporting, service journalism, and design covers the people, lifestyle, culture, entertainment, fashion, art and architecture, and news that define Southern California. Started in the spring of 1961, Los Angeles magazine has been addressing the needs and interests of our region for 48 years. The magazine continues to be the definitive resource for an affluent population that is intensely interested in a lifestyle that is uniquely Southern Californian.

2003 silverado radio wiring diagram: Los Angeles Magazine , 2003-11 Los Angeles magazine is a regional magazine of national stature. Our combination of award-winning feature writing, investigative reporting, service journalism, and design covers the people, lifestyle, culture, entertainment, fashion, art and architecture, and news that define Southern California. Started in the spring of 1961, Los Angeles magazine has been addressing the needs and interests of our region for 48 years. The magazine continues to be the definitive resource for an affluent population that is intensely interested in a lifestyle that is uniquely Southern Californian.

2003 silverado radio wiring diagram: Automotive News ,

2003 silverado radio wiring diagram: New York State Contract Reporter , 2000-11-06

2003 silverado radio wiring diagram: Standard Catalog of 4 X 4's Robert C. Ackerson, 1993 This comprehensive guide covers American four-wheel drive vehicles including trucks, vans, and sport utility vehicles. Updated information includes AMC, Chevrolet, Dodge, Ford, Jeep, International Scout, GMC, and other manufacturers. All 4x4 enthusiasts will find everything they

need to know about their favorite vehicle including identification and model numbers, body types, production totals, and other specifications.

2003 silverado radio wiring diagram: [Directory of United States Importers](#) , 2009 A list of U.S. importers and the products they import. The main company listing is geographic by state while products are listed by Harmonized Commodity Codes. There are also alphabetical company and product indexes.

2003 silverado radio wiring diagram: **California Services Register** , 1990

2003 silverado radio wiring diagram: [IEEE Membership Directory](#) Institute of Electrical and Electronics Engineers, 1979

2003 silverado radio wiring diagram: *Publishers, Distributors & Wholesalers of the United States* R.R. Bowker company, 2003

2003 silverado radio wiring diagram: **Who's who in America** , 2003

Related to 2003 silverado radio wiring diagram

2003 - Wikipedia The year 2003 was marked by the invasion of Iraq and the subsequent period of occupation and insurgency. The Kashmir conflict also saw a period of escalation, and the Second Intifada

What Happened in 2003 - On This Day What happened and who was famous in 2003? Browse important and historic events, world leaders, famous birthdays and notable deaths from the year 2003

Major Events of 2003 - Historical Moments That Defined the Year Discover the most significant events of 2003, from world-changing political decisions to cultural milestones. Explore the key moments that shaped history during this

2003 major events | Future Timeline Major events of 2003 – a timeline of business, politics, technology, and other notable events of the year 2003

2003 Archives | HISTORY On December 17, 2003, *The Lord of the Rings: The Return of the King*, the final film in the trilogy based on the best-selling fantasy novels by J.R.R. Tolkien, opens in theaters

What Happened In 2003 - Historical Events 2003 - EventsHistory What happened in the year 2003 in history? Famous historical events that shook and changed the world. Discover events in 2003

Top News Stories from 2003 - Infoplease *The Lord of the Rings: The Return of the King* not only dominated the 2003 box office, but it also led the way in Oscar nominations. The Matrix fans were treated to two sequels: Matrix:

2003 Annual History Facts - History in Popular Culture Rock band Green Day finished an album in 2003, but was never released because the master tracks were stolen from the studio. Instead of re-recording the album, the band

2003 in the United States - Wikipedia The Florida Marlins defeat the New York Yankees in six games in the 2003 World Series to win their second World Series title. The Cedar Fire begins in San Diego County, burning 280,000

Timeline: 2003 - Everything That Happened In The Year 2003 The year that gave us all kinds of weird - the North Korean Nuclear treaty withdrawal (gulp), 50 Cent's debut album 'Get Rich or Die Tryin', the sad loss of 'the old man' rock formation in New

2003 - Wikipedia The year 2003 was marked by the invasion of Iraq and the subsequent period of occupation and insurgency. The Kashmir conflict also saw a period of escalation, and the Second Intifada

What Happened in 2003 - On This Day What happened and who was famous in 2003? Browse important and historic events, world leaders, famous birthdays and notable deaths from the year 2003

Major Events of 2003 - Historical Moments That Defined the Year Discover the most significant events of 2003, from world-changing political decisions to cultural milestones. Explore

the key moments that shaped history during this

2003 major events | Future Timeline Major events of 2003 – a timeline of business, politics, technology, and other notable events of the year 2003

2003 Archives | HISTORY On December 17, 2003, The Lord of the Rings: The Return of the King, the final film in the trilogy based on the best-selling fantasy novels by J.R.R. Tolkien, opens in theaters

What Happened In 2003 - Historical Events 2003 - EventsHistory What happened in the year 2003 in history? Famous historical events that shook and changed the world. Discover events in 2003

Top News Stories from 2003 - Infoplease The Lord of the Rings: The Return of the King not only dominated the 2003 box office, but it also led the way in Oscar nominations. The Matrix fans were treated to two sequels: Matrix:

2003 Annual History Facts - History in Popular Culture Rock band Green Day finished an album in 2003, but was never released because the master tracks were stolen from the studio. Instead of re-recording the album, the band

2003 in the United States - Wikipedia The Florida Marlins defeat the New York Yankees in six games in the 2003 World Series to win their second World Series title. The Cedar Fire begins in San Diego County, burning 280,000

Timeline: 2003 - Everything That Happened In The Year 2003 The year that gave us all kinds of weird - the North Korean Nuclear treaty withdrawal (gulp), 50 Cent's debut album 'Get Rich or Die Tryin', the sad loss of 'the old man' rock formation in New

Back to Home: <https://lxc.avoicemen.com>